

# CHAPTER 2

## BASIC LAWS


### QUESTION 2.1

A metal wire has a uniform cross-section  $A$ , length  $l$ , and resistance  $R$  between its two end points. It is uniformly stretched so that its length becomes  $\alpha l$ . The new resistance is

- (A)  $\alpha R$
- (B)  $\alpha^2 R$
- (C)  $\sqrt{\alpha} R$
- (D)  $e^\alpha R$
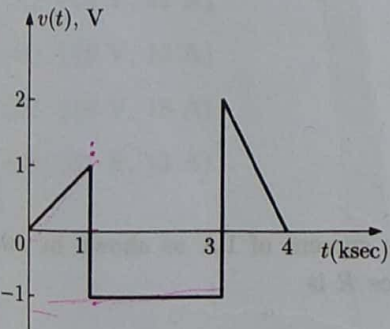
### QUESTION 2.2

The voltage across a  $100 \Omega$  resistor is sketched in the figure. The energy delivered to the resistor from  $t = 0$  to  $t = 2$  msec will be




### QUESTION 2.3

When a resistor  $R$  is connected to a current source it consumes a power of 18 W. When the same  $R$  is connected to a voltage source having the same magnitude as the current source, the power absorbed by  $R$  is 45 W. The magnitude of the current source and the value of  $R$  are

- (A)  $\sqrt{18}$  A and  $1 \Omega$
- (B) 3 A and  $2 \Omega$
- (C) 1 A and  $18 \Omega$
- (D) 6 A and  $0.5 \Omega$

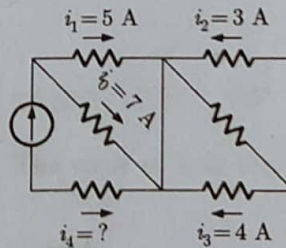
### QUESTION 2.4

The current  $i_4$  in the circuit of the figure is equal to




- (A) 12 A
- (B) -12 A
- (C) 4 A
- (D) None of these

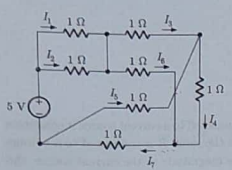**QUESTION 2.5**  
Which one of the following equations is valid for the circuit shown below?




- (A)  $I_5 + I_6 - I_7 = 0$
- (B)  $I_5 - I_6 + I_7 = 0$
- (C)  $I_5 + I_6 + I_7 = 0$
- (D)  $I_5 + I_6 - I_7 = 0$

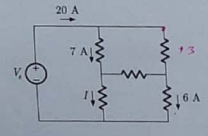**QUESTION 2.6**  
In the circuit shown in figure, unknown current  $I$  is




----- Amp

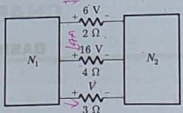**QUESTION 2.7**  
The two electrical networks  $N_1$  and  $N_2$  are connected through three resistors as shown in figure. The voltage across  $3\ \Omega$  resistor is




----- Volts

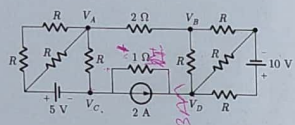**QUESTION 2.8**  
If  $V_A - V_B = 6\text{ V}$  then  $V_C - V_D$  is




- (A)  $-5\text{ V}$
- (B)  $2\text{ V}$
- (C)  $3\text{ V}$
- (D)  $6\text{ V}$

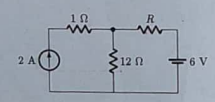**QUESTION 2.9**  
If the  $12\ \Omega$  resistor draws a current of  $1\text{ A}$  as shown in the figure, the value of resistance  $R$  is




- (A)  $4\ \Omega$
- (B)  $6\ \Omega$
- (C)  $8\ \Omega$
- (D)  $18\ \Omega$

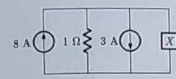**QUESTION 2.10**  
Consider the circuit shown in figure below. Let  $X$  be a  $4\ \Omega$  resistor then power absorbed by  $X$  is  $P_1$  and when  $X$  be a  $6\text{ V}$  independent voltage source with positive terminal at top, then power absorbed by  $X$  is  $P_2$ . What is the value of  $P_1/P_2$ ?




- (A)  $3\text{ V}$
- (B)  $-3\text{ V}$
- (C)  $5\text{ V}$
- (D) None of these

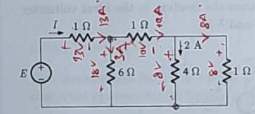**QUESTION 2.11**  
The values of  $E$  and  $I$  for the circuit shown in figure are




- (A)  $(13\text{ V}, 31\text{ A})$
- (B)  $(18\text{ V}, 13\text{ A})$
- (C)  $(18\text{ V}, 18\text{ A})$
- (D)  $(31\text{ V}, 13\text{ A})$

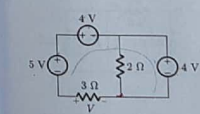**QUESTION 2.12**  
The voltage  $V$  in the figure equal to



$-4 - 4 + 5 + V = 0$   
 $V = 3$

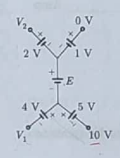
**QUESTION 2.13**  
In the given circuit, the value of the voltage source  $E$  is



- (A)  $-16\text{ V}$
- (B)  $4\text{ V}$
- (C)  $-6\text{ V}$
- (D)  $16\text{ V}$

$10 + 5 + E + 1 = 0$   
 $E = -16\text{ V}$   
 $0 - 1 + 2 = V$   
 $V = 1$   
 $10 + 5 - 4 = V$   
 $V = 11$

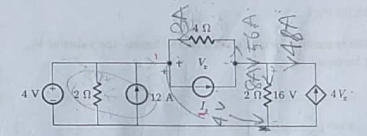
**QUESTION 2.14**  
The value of  $I$  in the following circuit is equal to



----- Amp

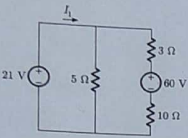QUESTION 2.15


In the following circuit, what is the value of current  $I_1$ ?



----- Amp

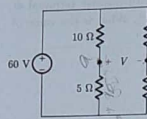QUESTION 2.18


The voltage  $V$  in the following circuit, equals to



----- Volt

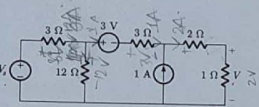QUESTION 2.16


If  $V = 2$  V in the circuit below, then value of  $V_1$  equals to



----- Volt

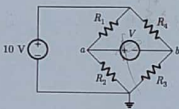QUESTION 2.19


If  $R_1 = R_2 = R_3 = R$  and  $R_4 = 1.1R$  in the bridge circuit shown in the figure, then the reading in the ideal voltmeter connected between  $a$  and  $b$  is



----- V

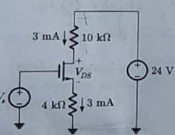QUESTION 2.17


In the transistor circuit shown in the figure, the value of  $V_{DS}$  will be equal to



----- Volt

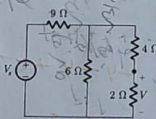QUESTION 2.20

If  $V = 3$  V in the circuit of figure, then  $V_1$  is equal to




----- Volt

QUESTION 2.21

How many 200 W/220 V incandescent lamps connected in series would consume that same total power as a single 100 W/220 V incandescent lamp?

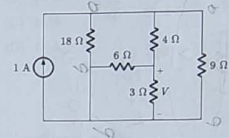QUESTION 2.25

In the resistive network shown below the value of voltage  $V$  is



----- Volt


QUESTION 2.22

A 100 ohm, 1 W resistor and a 800 ohm, 2 W resistor are connected in series. The maximum dc voltage that can be applied continuously to the series circuit without exceeding the power limit of any of the resistors is

----- V

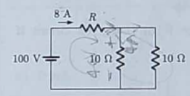QUESTION 2.26

In the figure given below the value of  $R$  is



- (A) 2.5 ohm
- (B) 5.0 ohm
- (C) 7.5 ohm
- (D) 10.0 ohm


QUESTION 2.23

Two incandescent light bulbs of 40 W and 60 W rating are connected in series across the mains. Then

- (A) the bulbs together consume 100 W
- (B) the bulbs together consume 50 W
- (C) the 60 W bulb glows brighter
- (D) the 40 W bulb glows brighter

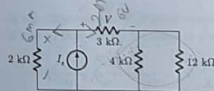QUESTION 2.24


For the circuit shown below it is given that  $V = 6$  volt, then what is the value of  $I_1$ ?



----- mA

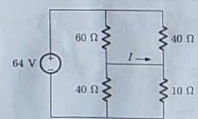
QUESTION 2.27

The value of current  $I$  in the circuit below is equal to




----- Amp

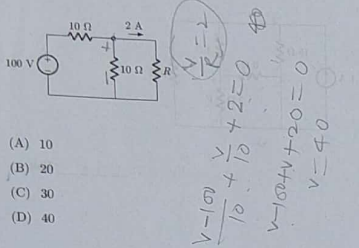**QUESTION 2.28**  
In figure, the value of resistance  $R$  in  $\Omega$  is




- (A) 10
- (B) 20
- (C) 30
- (D) 40

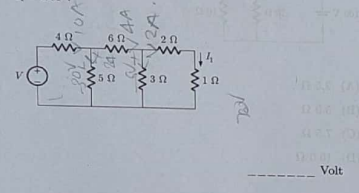**QUESTION 2.29**  
What is the value of voltage  $V$  in the given circuit if  $I_1 = 2$  A?




- (A) 10 V
- (B) 15 V
- (C) 5 V
- (D) None of the above

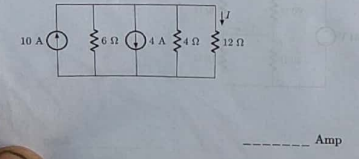**QUESTION 2.30**  
In the circuit shown below, the current  $I$  is equal to




\_\_\_\_\_ Amp

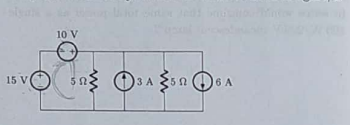**QUESTION 2.31**  
The power absorbed by each of  $5\Omega$  resistor shown in figure, is \_\_\_\_\_ Watts




\_\_\_\_\_ Watts

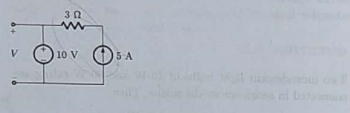**QUESTION 2.32**  
The voltage  $V$  in the figure is



- (A) 10 V
- (B) 15 V
- (C) 5 V
- (D) None of the above

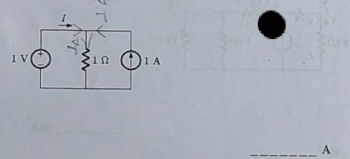**QUESTION 2.33**  
The current  $I$  supplied by the dc voltage source in the circuit shown below is



\_\_\_\_\_ A


**QUESTION 2.34**  
Assuming ideal elements in the circuit shown below, the voltage  $V_{ab}$  will be



\_\_\_\_\_ V


- Which of the following can be the value of the current source  $I$ ?
- (A) 10 A
  - (B) 13 A
  - (C) 15 A
  - (D) 18 A

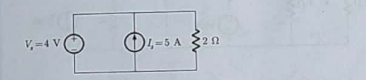**QUESTION 2.35**  
For the circuit shown, find out the current flowing through the  $2\Omega$  resistance. Also identify the changes to be made to double the current through the  $2\Omega$  resistance.




- (A) (5 A; Put  $V_s = 30$  V)
- (B) (2 A; Put  $V_s = 8$  V)
- (C) (5 A; Put  $I_s = 10$  A)
- (D) (7 A; Put  $I_s = 12$  A)

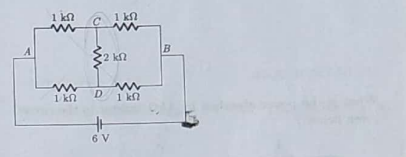**QUESTION 2.37**  
The current through the  $2\text{ k}\Omega$  resistance in the circuit shown is




- (A) 0 mA
- (B) 1 mA
- (C) 2 mA
- (D) 6 mA

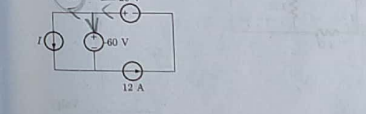**QUESTION 2.36**  
In the interconnection of ideal sources shown in the figure, it is known that the  $60$  V source is absorbing power.



\_\_\_\_\_ Volts

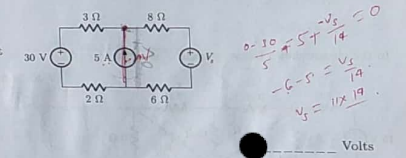
**QUESTION 2.38**  
In the circuit shown below the  $5$  A source supplies no power, the value of source  $V_s$  is



\_\_\_\_\_ Volts

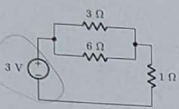QUESTION 2.39


The power supplied by the dc voltage source in the circuit shown below is



----- W

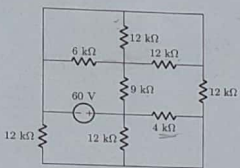QUESTION 2.40


What is the power absorbed by 4 kΩ resistor in the circuit given below ?



----- mW

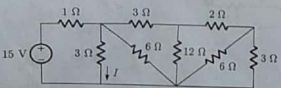QUESTION 2.41


In the circuit shown below, current I is equal to



----- Amp

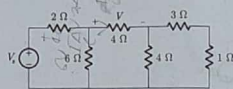QUESTION 2.42


In the circuit below if V = 4 volt, then V<sub>1</sub> is



----- Volts

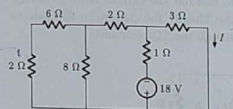QUESTION 2.43


What is the value of current I in the circuit below ?



----- Amp

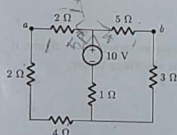QUESTION 2.44


In the figure, the potential difference between point a and b is



----- Volt

QUESTION 2.45

In the circuit of figure, the value of k such that power dissipated by 4 Ω resistor is 5184 W, will be

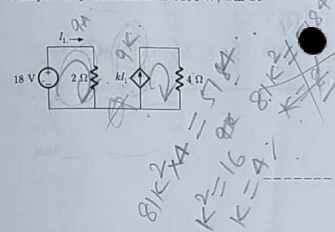


QUESTION 2.48

For the given circuit, what value of k will produce voltage gain V<sub>2</sub>/V<sub>1</sub> = -10 ?




QUESTION 2.46

In the following circuit, the value of R that is required to deliver a power of 160 kW to the 16 Ω resistor would be

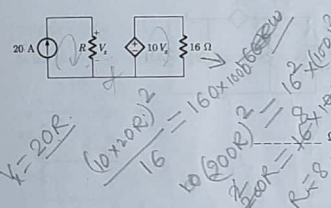

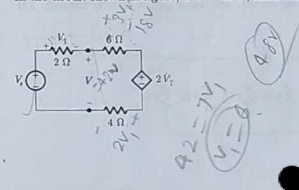QUESTION 2.49


In the circuit shown in figure, if V = 42 V, then value of V<sub>1</sub> is



----- Volt


QUESTION 2.47

In the following circuit, power dissipated by 5 Ω resistor is 20 W. What is the values of source voltage V<sub>1</sub> ?

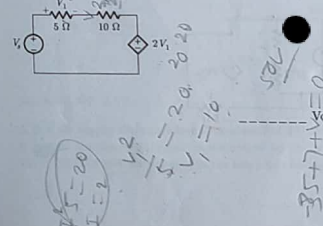

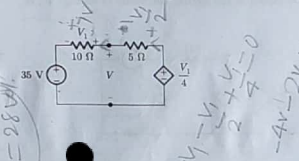QUESTION 2.50


For the circuit shown in figure, what is the voltage V



----- Volt

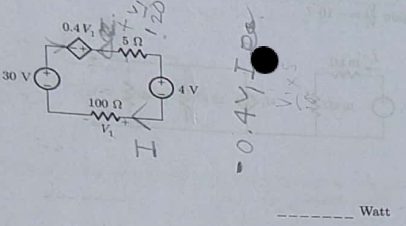**QUESTION 2.51**


How much power is absorbed by the dependent source in the following circuit?



\_\_\_\_\_ Watt

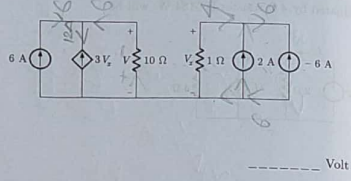**QUESTION 2.54**


In the following circuit, voltage  $V$  across  $10\Omega$  resistor is \_\_\_\_\_ Volt



\_\_\_\_\_ Volt

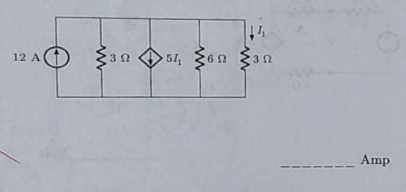**QUESTION 2.52**


In the given circuit, the value of current  $I_1$  through  $3\Omega$  resistor is \_\_\_\_\_ Amp



\_\_\_\_\_ Amp

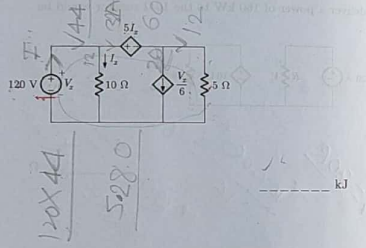**QUESTION 2.55**


What is the power delivered by the 120 V source in the given circuit? \_\_\_\_\_ kJ



\_\_\_\_\_ kJ

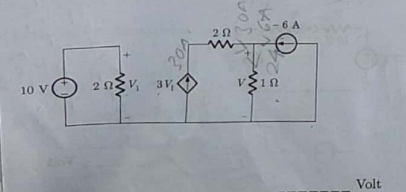**QUESTION 2.53**


In the circuit shown in the figure, the value of voltage  $V$ , is \_\_\_\_\_ Volt



\_\_\_\_\_ Volt

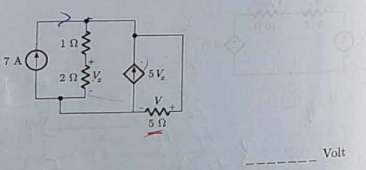**QUESTION 2.56**


What is the voltage  $V$  across the  $5\Omega$  resistor shown below? \_\_\_\_\_ Volt



\_\_\_\_\_ Volt

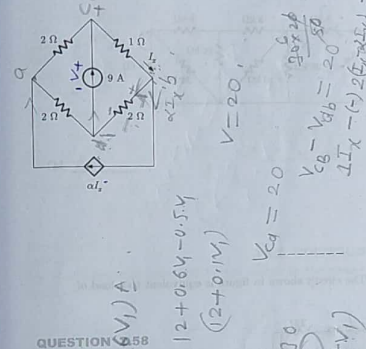**QUESTION 2.57**


The value of  $\alpha$  in the network such that power supplied by 9 A source is 180 W, will be equal to \_\_\_\_\_



\_\_\_\_\_

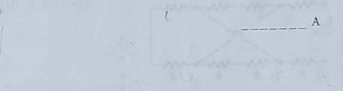**QUESTION 2.60**


A 10 V battery with an internal resistance of  $1\Omega$  is connected across a nonlinear load whose  $V-I$  characteristic is given by  $7I = V^2 + 2V$ . The current delivered by the battery is \_\_\_\_\_ A



\_\_\_\_\_ A

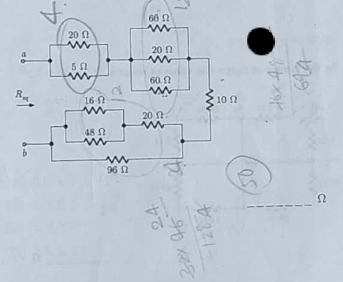**QUESTION 2.61**


What is the equivalent resistance  $R_{eq}$  looking into terminal a-b of the following network? \_\_\_\_\_  $\Omega$



\_\_\_\_\_  $\Omega$

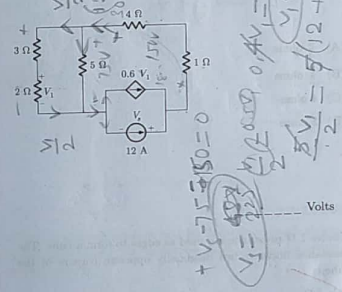**QUESTION 2.58**

In the given circuit, voltage  $V_1$  across current source is \_\_\_\_\_ Volts




\_\_\_\_\_ Volts

**QUESTION 2.59**

A 3 V dc supply with an internal resistance of  $2\Omega$  supplies a passive non-linear resistance characterized by the relation  $V_{NL} = I_{NL}^2$ . The power dissipated in the non linear resistance is \_\_\_\_\_ W

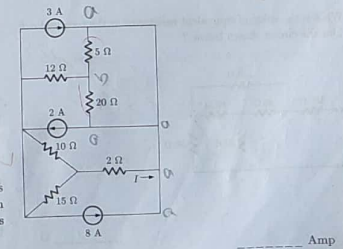**QUESTION 2.62**


For the given circuit, the value of current  $I$  equals to \_\_\_\_\_ Amp



\_\_\_\_\_ Amp

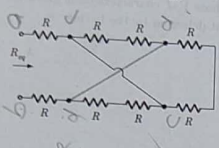QUESTION 2.63


In the following network  $\frac{R_{eq}}{R}$  is equal to



Handwritten solution:  $2R + 2R = 4R$ ,  $\frac{4R}{3} = \frac{4}{3}R$ ,  $\frac{4R}{3} \div R = \frac{4}{3} = 1.33$

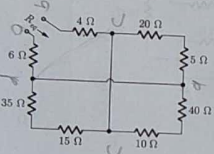QUESTION 2.64


In the circuit of figure the value of resistor  $R_{eq}$  is



Handwritten solution:  $22.5 \Omega$

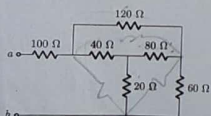QUESTION 2.65


What is the value of equivalent resistance at the terminal a-b for the circuit shown below?



Blank space for answer

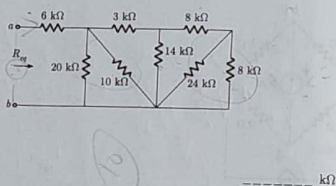QUESTION 2.66


What is the value of equivalent resistance  $R_{eq}$  between terminal a-b in the following network?



Handwritten solution:  $10 k\Omega$

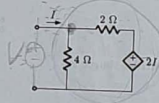QUESTION 2.67

The circuit shown in figure is equivalent to a load of



- (A)  $\frac{4}{3}$  ohms
- (B)  $\frac{8}{3}$  ohms
- (C) 4 ohms
- (D) 2 ohms

Handwritten solution:  $V = 2V$ ,  $V = 2V - 4V = -2V$ ,  $3V = 8V$ ,  $2V = 8V$


QUESTION 2.68

Twelve  $1 \Omega$  resistance are used as edges to form a cube. The resistance between two diagonally opposite corners of the cube is

- (A)  $\frac{5}{6} \Omega$
- (B)  $1 \Omega$
- (C)  $\frac{3}{2} \Omega$
- (D)  $\frac{3}{4} \Omega$

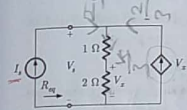QUESTION 2.69

What is the equivalent resistance  $R_{eq}$  seen by the current source  $I_s$  in the circuit?




Handwritten solution:  $V_s = 11V$ ,  $V_s = 11V$ ,  $V_s = 11V$ ,  $V_s = 11V$

- (A) 1.5, 3 and 9
- (B) 3, 9 and 1.5
- (C) 9, 3 and 1.5
- (D) 3, 1.5 and 9

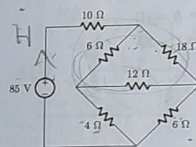
QUESTION 2.70

How much power is generated by the source in the given network?



Handwritten solution:  $P = 285 \text{ W}$ ,  $85 \text{ V}$ ,  $3.35 \text{ A}$

- (A) 2.5, 5, 5
- (B) 5, 2.5, 5
- (C) 5, 5, 2.5
- (D) 2.5, 5, 2.5

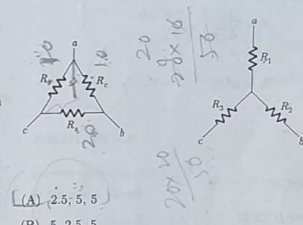


QUESTION 2.72

In figure,  $R_1$ ,  $R_2$  and  $R_3$  are  $20 \Omega$ ,  $20 \Omega$  and  $10 \Omega$  respectively. The resistances  $R_1$ ,  $R_2$  and  $R_3$  in  $\Omega$  of an equivalent star connection are

Handwritten solution:  $20, 10, 10$

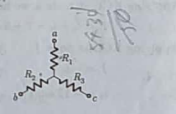QUESTION 2.71

A Delta-connected network with its Wye-equivalent is shown in the given figure. The resistance  $R_1$ ,  $R_2$  and  $R_3$  (in ohms) are respectively



Handwritten solution:  $5, 30, 15$

# SOLUTIONS

ON 2.1

tion is (B).

$$R = \frac{\rho l}{A}$$

nt volume,

$$R = \frac{\rho l}{A} \times \frac{l}{l} = \frac{\rho l^2}{V}$$

$$R \propto l^2$$

$$R_2 = \alpha^2 R_1$$

ON 2.2

swer is 13.33.

$$p(t) = \frac{v^2(t)}{R}$$

$$E[0, t] = \int_0^t p(t) dt = \frac{1}{100} \int_0^t v^2(t) dt$$

$$\text{Graph } v(t) = \begin{cases} t, & 0 \leq t < 1 \text{ ksec} \\ -1, & 1 \leq t < 2 \text{ ksec} \end{cases}$$

$$E[2] = \frac{1}{100} \int_0^2 v^2(t) dt$$

$$= \frac{1}{100} \int_0^1 v^2(t) dt + \frac{1}{100} \int_1^2 v^2(t) dt$$

$$= \frac{1}{100} \int_0^1 t^2 dt + \frac{1}{100} \int_1^2 (-1)^2 dt$$

$$= \frac{1}{100} \left[ \frac{t^3}{3} \right]_0^1 + \frac{1}{100} [t]_1^2$$

$$= \frac{1}{100} \left[ \frac{1 \times 10^3}{3} - 0 \right] + \frac{1}{100} [2 \times 10^3 - 1 \times 10^3]$$

$$= \frac{10}{3} + 10$$

$$= \frac{40}{3} = 13.33 \text{ Joule}$$

## SOLUTION 2.3

Correct option is (B).

When  $R$  is connected to current source power absorbed by  $R$  is

$$P_1 = I^2 R = 18 \text{ W},$$

$I$  → value of current source

When  $R$  is connected to voltage source power absorbed is

$$P_2 = \frac{V^2}{R} = 4.5 \text{ W},$$

$V$  → value of voltage source

Given that  $I$  and  $V$  are same in magnitude, so dividing above two

$$\frac{I^2 R}{V^2/R} = \frac{18}{4.5}$$


$$R^2 = 20 \Rightarrow R = 2 \Omega$$

$$I^2 \times 2 = 18 \Rightarrow I_s = 3 \text{ A}$$

## SOLUTION 2.4

Correct option is (B).

The given figure is shown below.

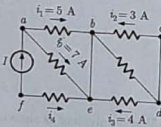

Applying KCL at node  $a$  we have

$$I = i_6 + i_1 = 7 + 5 = 12 \text{ A}$$

Applying KCL at node  $f$

$$I = -i_4$$

So,  $i_4 = -12 \text{ amp}$

## SOLUTION 2.5

Correct option is (D).

Writing KCL at top right node

$$I_3 + I_5 = I_4$$

...(i)

KCL at bottom right node

$$I_4 + I_6 = I_7$$

$$I_4 = I_7 - I_6$$

Substituting  $I_4$  into equation (i)

$$I_3 + I_5 = I_7 - I_6$$

$$I_3 + I_5 + I_6 - I_7 = 0$$

NOTE :

The problem can be solved in a single step using KCL at bottom node.

## SOLUTION 2.7

Correct answer is -21.

Algebraic sum of the current entering or leaving a cutset is equal to 0.

$$I_{5\Omega} + I_{1\Omega} + I_{3\Omega} = 0$$

$$\frac{6}{2} + \frac{16}{4} + I_{5\Omega} = 0$$


$$I_{5\Omega} = -7 \text{ A}$$

$$V_{5\Omega} = -7 \times 3 = -21 \text{ V}$$
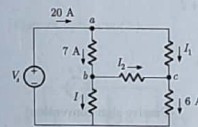
## SOLUTION 2.6

Correct answer is 14.

Consider the circuit with unknown current and reference direction as shown below



Applying KCL at node 'a'

$$\Sigma I_{\text{entering}} = \Sigma I_{\text{leaving}}$$

$$20 = 7 + I_1$$

$$I_1 = 20 - 7 = 13 \text{ A}$$

Applying KCL at node 'c'

$$\Sigma I_{\text{entering}} = \Sigma I_{\text{leaving}}$$

$$I_1 + I_2 = 6$$

$$I_2 = 6 - I_1 = 6 - 13$$

$$= -7 \text{ A}$$

Applying KCL at node 'b'

$$\Sigma I_{\text{entering}} = \Sigma I_{\text{leaving}}$$

$$7 = I + I_2$$

$$7 = I - 7$$

$$I = 7 + 7 = 14 \text{ A}$$

## SOLUTION 2.8

Correct option is (A).


In the given circuit

$$V_A - V_B = 6 \text{ V}$$

So current in the branch will be

$$I_{AB} = \frac{6}{2} = 3 \text{ A}$$

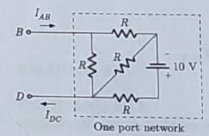
We can see, that the circuit is a one port circuit looking from terminal  $BD$  as shown below



For a one port network current entering one terminal, equals the current leaving the second terminal. Thus the outgoing current from  $A$  to  $B$  will be equal to the incoming current from  $D$  to  $C$  as shown
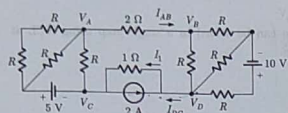
$$\text{i.e. } I_{DC} = I_{AB} = 3 \text{ A}$$






The total current in the resistor 1Ω will be  
 $I_1 = 2 + I_{DC}$  (Writing KCL at node D)  
 $= 2 + 3 = 5 \text{ A}$   
 So,  $V_{CD} = 1 \times (-I_1) = -5 \text{ V}$

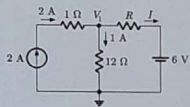**SOLUTION 2.9**


Correct option is (B).  
 The circuit is as given below.




Voltage across 12Ω resistor  
 $V_1 = 12 \times 1 = 12 \text{ V}$   
 Using KCL at top center node  
 $2 = 1 + I$   
 $I = 1 \text{ A}$   
 $I = \frac{V_1 - 6}{R} = 1$   
 $12 - 6 = R$   
 $R = 6 \Omega$

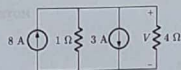**SOLUTION 2.10**

Correct answer is -0.667.  
 $X : 4 \Omega$  resistance



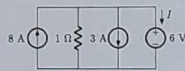
Applying KCL at the top node  
 $8 = 3 + \frac{V}{1} + \frac{V}{4}$   
 $5 = \frac{5}{4}V \Rightarrow V = 4 \text{ volt}$   
 Power absorbed by X  
 $P_1 = \frac{(V)^2}{R} = \frac{(4)^2}{4} = 4 \text{ W}$   
 $X : 6 \text{ V}$  independent source, with +ve terminal at top



Applying KCL at the top node  
 $8 = \frac{6}{1} + 3 + I$   
 $I = -1 \text{ A}$   
 Power absorbed by 6V source  
 $P_2 = (-1) \times (6)$   
 $= -6 \text{ W}$  (Passive sign convention)  
 $\frac{P_1}{P_2} = \frac{4}{-6} = -\frac{2}{3} = -0.667$

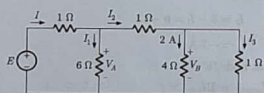
**SOLUTION 2.11**

Correct option is (D).  
 Solving the circuit




Voltage across 4Ω,  
 $V_0 = 4 \times 2 = 8 \text{ V}$

Current in 1Ω,  
 $I_3 = \frac{V_0}{1\Omega} = \frac{8}{1} = 8 \text{ A}$   
 Using KCL,  
 $I_2 = I_3 + 2 = 8 + 2 = 10 \text{ A}$   
 So,  $V_1 = I_2 \times 1 + V_0$  (KVL in the middle loop)  
 $= 10 + 8 = 18 \text{ V}$   
 Current in 6Ω,  
 $I_1 = \frac{V_1}{6} = \frac{18}{6} = 3 \text{ A}$   
 Using KCL,  $I = I_1 + I_2 = 3 + 10 = 13 \text{ A}$   
 Using Ohm's Law current in left most 1Ω is given by  
 $\frac{E - V_1}{1} = I$   
 $E - 18 = 13 \times 1$   
 $E = 31 \text{ V}$

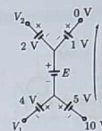

**SOLUTION 2.12**

Correct option is (A).

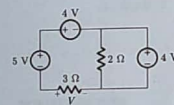


Writing KVL in the left mesh  
 $5 - 4 - 4 + V = 0$   
 $V = 3 \text{ V}$

**SOLUTION 2.13**

Correct option is (A).  
 Applying KVL in the right most loop starting from 10 V and going towards 0 V as shown in figure,  
 $10 + 5 + E + 1 = 0$   
 or  $E = -16 \text{ V}$

**SOLUTION 2.14**


Correct answer is 59.

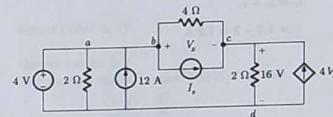

Applying KVL around the loop abcda  
 $4 - V_1 - 16 = 0$   
 $V_1 = -12 \text{ V}$   
 Applying KCL at node c  
 $4V_2 + I_1 + \frac{V_2}{4} = \frac{16}{2}$   
 $4(-12) + I_1 + \frac{(-12)}{4} = 8$   
 $I_1 - 48 - 3 = 8$  or  $I_1 = 59 \text{ A}$

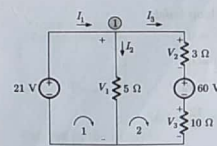**SOLUTION 2.15**


Correct answer is 1.2.  
 Consider the circuit as shown below



Applying KVL around Loop 1  
 $21 - V_1 = 0$   
 $V_1 = 21$  volt  
 Current  $I_3 = \frac{V_1}{5} = \frac{21}{5} = 4.2$  A (Ohm's Law)  
 Applying KVL around Loop 2  
 $V_1 - V_2 - 60 - V_3 = 0$  ... (1)  
 $V_2 = 3I_3, V_3 = 10I_3$  (Ohm's law)  
 Substituting  $V_1, V_2$  and  $V_3$  into equation (1), we get  
 $21 - 3I_3 - 60 - 10I_3 = 0$   
 $I_3 = -3$  A

Applying KCL at node 1,  
 $I_1 = I_2 + I_3$   
 $= 4.2 - 3 = 1.2$  A

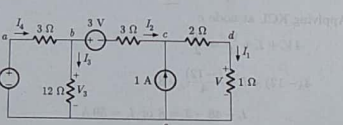**SOLUTION 2.16**  
 Correct answer is 18.  
 Consider the following currents and voltages in the circuit




$I_1 = \frac{V}{1} = 2$  A  
 Applying KCL at node c  
 $I_3 + 1 = I_1$   
 $I_3 + 1 = 2$   
 $I_3 = 2 - 1 = 1$  A  
 Applying KVL around the loop bcdcb  
 $V_3 - 3 - 3I_3 - 2I_1 - 1I_1 = 0$   
 $V_3 - 3 - 3(1) - 2(2) - 1(2) = 0$   
 $V_3 - 12 = 0 \Rightarrow V_3 = 12$  V  
 $I_3 = \frac{V_3}{12} = \frac{12}{12} = 1$  A  
 Applying KCL at node b

$I_4 = I_2 + I_3$   
 $I_4 = 1 + 1 = 2$  A  
 Applying KVL around the loop abea  
 $V_4 - 3I_4 - V_2 = 0$   
 $V_4 = 3(2) + 12 = 18$  V  
 (( $I_4 = 2$  A,  $V_3 = 12$  V))



**SOLUTION 2.17**  
 Correct answer is 18.  
 In the given circuit we do not know the current voltage characteristic of the transistor, but it still obeys both KCL and KVL. Applying KVL around the outer loop,  
 $24 - (10 \times 10^3)(3 \times 10^{-3}) - V_{DS} = 0$   
 $-(4 \times 10^3)(3 \times 10^{-3}) = 0$   
 $24 - 30 - V_{DS} - 12 = 0$   
 $V_{DS} = 18$  V

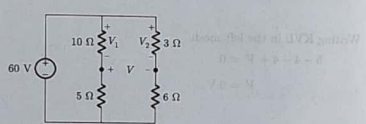**SOLUTION 2.18**  
 Correct answer is -20.



Using voltage division  
 $V_1 = \frac{10}{10+5}(60) = 40$  V  
 $V_2 = \frac{3}{(6+3)}(60) = 20$  V  
 Applying KVL  
 $V + V_1 - V_2 = 0$   
 $V = -V_1 + V_2 = -40 + 20 = -20$  V

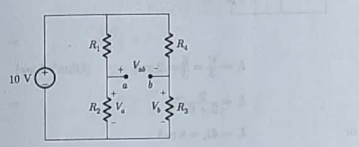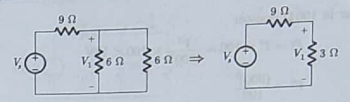**SOLUTION 2.19**  
 Correct answer is -0.238 V.  
 The circuit can be redrawn in a simpler way as shown below




$V_2 = \frac{R_3}{R_1 + R_2}(10)$  (Using voltage division)  
 $V_2 = 5$  V ( $R_1 = R_2$ )  
 Now,  $V_3 = \frac{R_3}{R_3 + R_4}(10)$  (Using voltage division)  
 $= \frac{1.1}{2.1} \times 10 = 5.238$  V  
 $V = V_{23} = V_2 - V_3 = 5 - 5.238 = -0.238$  V

Using voltage division  
 $V_1 = \frac{3}{9+3}(V_2) = \frac{V_2}{4}$   
 $V_2 = 4V_1 = 4 \times 9 = 36$  V ( $V_1 = 9$  volt)

**SOLUTION 2.21**  
 Correct answer is 2.  
 Resistance of the bulb rated 200 W/220 V is  
 $R_1 = \frac{V^2}{P_1} = \frac{(220)^2}{200} = 242 \Omega$   
 Resistance of 100 W/220 V lamp is  
 $R_2 = \frac{V^2}{P_2} = \frac{(220)^2}{100} = 484 \Omega$

To connect in series  
 $R_T = n \times R_1$   
 $484 = n \times 242$   
 $n = 2$

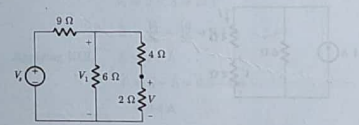**SOLUTION 2.20**  
 Correct answer is 36.  
 Let voltage across parallel branches is  $V_1$ , as shown in figure



Using voltage division  
 $V = \frac{2}{2+4}(V_1) = \frac{V_1}{3}$   
 $V_1 = 3 \times 3 = 9$  V ( $V = 3$  volt)  
 Combining resistances

**SOLUTION 2.22**  
 Correct answer is 45 V.



Current in the resistors  
 $I = \frac{V}{100+800} = \frac{V}{900}$

Power in 100 Ω resistor

$$P_1 = I^2 \times 100 = \frac{V^2}{(900)^2} \times 100 < 1 \text{ W}$$

$$V^2 < \frac{(900)^2}{100}$$

$$V^2 = 8100$$

$$V < 90 \text{ V}$$

Power in 800 Ω resistor


$$P_2 = I^2 \times 800 = \frac{V^2}{(900)^2} \times 800 < 2 \text{ W}$$

$$V^2 < \frac{2 \times (900)^2}{800}$$

$$V^2 < 2025$$

$$V < 45 \text{ V}$$

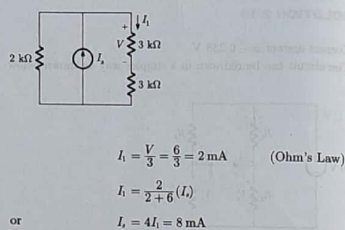The maximum voltage that can be applied will be 45 V.



$$I_1 = \frac{V}{3} = \frac{6}{3} = 2 \text{ mA} \quad (\text{Ohm's Law})$$

$$I_1 = \frac{2}{2+6} (I_s)$$


or

$$I_1 = 4I_s = 8 \text{ mA}$$

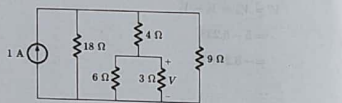**SOLUTION 2.25**

Correct answer is 1.


Rewriting the circuit in a simpler way, as shown



Combining the resistor combination

$$18 \Omega \parallel 9 \Omega = 6 \Omega$$
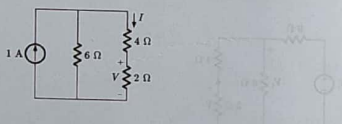
$$6 \Omega \parallel 3 \Omega = 2 \Omega$$



Using current division

$$I = \frac{6}{6+6} (1) = 0.5 \text{ A}$$

$$V = I \times 2 = 0.5 \times 2 = 1 \text{ V} \quad (\text{Ohm's Law})$$

**SOLUTION 2.23**

Correct option is (D).

Let resistance of 40 W and 60 W lamps are  $R_1$  and  $R_2$  respectively

$$P \propto \frac{1}{R^2}$$

$$\frac{P_1}{P_2} = \frac{R_2^2}{R_1^2}$$

$$\frac{R_2^2}{R_1^2} = \frac{40}{60}$$

$$R_2 < R_1$$

40 W bulb has high resistance than 60 W bulb, when connected in series power is

$$P_1 = I^2 R_1$$

$$P_2 = I^2 R_2$$

$$\therefore R_1 > R_2, \text{ So, } P_1 > P_2$$

therefore, 40 W bulb glows brighter.

**SOLUTION 2.24**

Correct answer is 8.

By combining 4 kΩ and 12 kΩ

$$4 \text{ k}\Omega \parallel 12 \text{ k}\Omega = 3 \text{ k}\Omega$$

**SOLUTION 2.26**

Correct option is (C).


Current in the circuit

$$I = \frac{100}{R + (10 \parallel 10)} = 8 \text{ A}$$

$$\Rightarrow \frac{100}{R+5} = 8$$

$$100 = 8R + 40$$
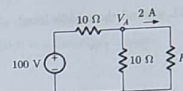
$$\Rightarrow R = \frac{60}{8} = 7.5 \Omega$$



$$\text{Voltage } V_A = \frac{(10 \parallel R)}{10 + (10 \parallel R)} (100)$$


$$= \frac{100}{10 + \frac{10R}{10+R}} \times \frac{10R}{10+R}$$

$$= \frac{1000R}{100 + 20R}$$

$$= \frac{50R}{5+R}$$

**SOLUTION 2.27**

Correct answer is 0.4.

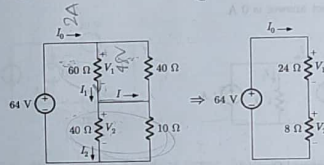

$$I_0 = \frac{64}{24+8} = 2 \text{ A}$$

$$V_1 = 2 \times 24 = 48 \text{ V}$$

$$I_1 = \frac{V_1}{60} = \frac{48}{60} = 0.8 \text{ A}$$

$$V_2 = 2 \times 8 = 16 \text{ V}$$

$$I_2 = \frac{V_2}{40} = \frac{16}{40} = 0.4 \text{ A}$$

$$I_1 = I + I_2$$

$$I = I_1 - I_2 = 0.8 - 0.4 = 0.4 \text{ A}$$

Applying KCL,

**SOLUTION 2.29**

Correct answer is 70.

We assume currents in each branch of the circuit as shown below.



We can see that  $I_3$  is divided into two equal parallel resistances 3 Ω each.

$$I_3 = I_1 + I_2$$

$$I_3 = 2I_1 = 2I_2 \quad (I_1 = I_2)$$

$$I_1 = 2 \times 2 = 4 \text{ A} \quad (I_1 = 2 \text{ A})$$

and

$$I_2 = \frac{I_3}{2} = \frac{4}{2} = 2 \text{ A}$$

$$V_{5\Omega} = V_{6\Omega} + V_{2\Omega}$$

**SOLUTION 2.28**

Correct option is (B).

In the circuit

(KVL around the middle loop)

$$= I_1 \times 6 + I_2 \times 3$$

$$= 4 \times 6 + 2 \times 3$$

$$= 24 + 6 = 30 \text{ V}$$

So  $I_1 = \frac{V_{5\Omega}}{5} = \frac{30}{5} = 6 \text{ A}$

$$I = I_1 + I_2$$

$$= 6 + 4 = 10 \text{ A}$$

(KCL)

$$V = 4I + 5I_1$$

(KVL around the left most loop)

$$= 4(10) + 5(6)$$

$$= 40 + 30 = 70 \text{ V}$$

Power absorbed by each of the 5 Ω resistor


$$P = \frac{(V)^2}{R} = \frac{(25)^2}{5} = 125 \text{ W}$$

**SOLUTION 2.32**

Correct option is (A).  
The voltage  $V$  is the voltage across voltage source and that is 10 V.

**SOLUTION 2.33**

Correct answer is 0 A.

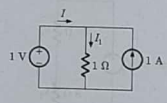

Current in 1 Ω resistor

$$I_1 = \frac{1}{1} = 1 \text{ A}$$

$$I + 1 = I_1$$

$$I = I_1 - 1 = 1 - 1 = 0 \text{ A}$$

(Using KCL)

**SOLUTION 2.34**

Correct answer is -3 Volt.  
Applying KVL in the circuit

$$V_{ab} - 2i + 5 = 0$$


$$V_{ab} = 2 \times 1 - 5$$

$$= -3 \text{ Volt}$$

$i = 1 \text{ A}$

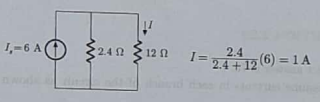**SOLUTION 2.30**


Correct answer is 1.  
Current sources are in parallel which is equivalent to  $I = 10 - 4 = 6 \text{ A}$  source.  $6 \Omega$  and  $4 \Omega$  resistors are in parallel, which is equivalent to  $2.4 \Omega$ .



$$I = \frac{2.4}{2.4 + 12} (6) = 1 \text{ A}$$

**SOLUTION 2.31**

Correct answer is 125.  
 $10 \text{ V}$  and  $15 \text{ V}$  voltage source are in series which is equivalent to  $15 + 10 = 25 \text{ V}$ .  $3 \text{ A}$  and  $6 \text{ A}$  current sources are in parallel and equivalent to  $6 - 3 = 3 \text{ A}$

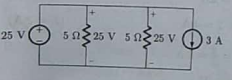

**SOLUTION 2.35**


Correct option is (B).  
Voltage across  $2 \Omega$  resistor,  
 $V_1 = 2 \text{ V}$

Current,  $I_{2\Omega} = \frac{V_1}{2} = \frac{2}{2} = 1 \text{ A}$

To make the current double we have to take  
 $V_1 = 8 \text{ V}$

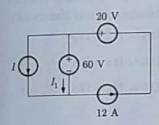**SOLUTION 2.36**


Correct option is (A).  
Circuit is as shown below



Since  $60 \text{ V}$  source is absorbing power. So, in  $60 \text{ V}$  source current flows from +ve to -ve direction  
So,  $I + I_1 = 12$  (KCL at the bottom left node)  
 $I = 12 - I_1$   
 $I$  is always less than  $12 \text{ A}$  So, only option (A) satisfies this conditions.

**SOLUTION 2.37**



Correct option is (A).

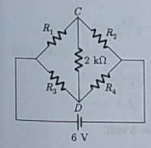

In the bridge,  $R_1 R_3 = R_2 R_4 = 1$   
So it is a balanced bridge,

**SOLUTION 2.38**

Correct answer is -154.

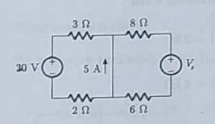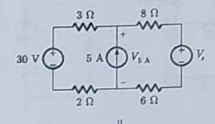

$$P_{5A} = 0 = V_{5A} \times 6 = 0 \Rightarrow V_{5A} = 0$$

So voltage across  $5 \text{ A}$  source is zero.  
Applying KCL at the top center node  
 $\frac{30}{3+2} + 5 + \frac{V_1}{8+6} = 0$   
 $\frac{30}{5} + 5 + \frac{V_1}{14} = 0$  or  $V_1 = -154 \text{ V}$   
 $I = 0 \text{ mA}$

**SOLUTION 2.39**


Correct answer is 3 W.

Total resistance seen by source  
 $R = (3 \Omega || 6 \Omega) + 1 \Omega$   
 $= 2 \Omega + 1 \Omega = 3 \Omega$


Power supplied by source,  
 $P_s = \frac{(3\text{V})^2}{R} = \frac{(3\text{V})^2}{3} = 3 \text{ W}$

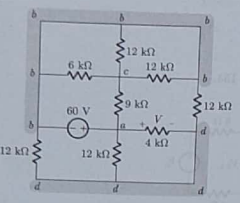**SOLUTION 2.40**

Correct answer is 100.  
We assign nodes a, b, c and d as shown below



Simplifying the circuit in following steps  
Between nodes c and b  
 $6\text{ k}\Omega \parallel 12\text{ k}\Omega \parallel 12\text{ k}\Omega = 3\text{ k}\Omega$   
Between nodes b and d  
 $12\text{ k}\Omega \parallel 12\text{ k}\Omega = 6\text{ k}\Omega$   
Between nodes a and d  
 $4\text{ k}\Omega \parallel 12\text{ k}\Omega = 3\text{ k}\Omega$   
Between node c and a, 9 kΩ resistor is connected.

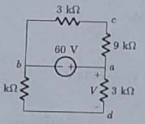


Using voltage division  
 $V = \frac{3}{3+6}(60) = 20\text{ V}$   
Power absorbed by 4 kΩ resistor  
 $P = \frac{V^2}{R} = \frac{(20)^2}{4 \times 10^3} = \frac{400}{4 \times 10^3} = 100\text{ mW}$

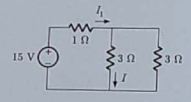**SOLUTION 2.41**

Correct answer is 3.  
Simplifying the resistor combination as shown below. Starting from the right most resistors

$$\begin{aligned} 6\ \Omega \parallel 3\ \Omega &= 2\ \Omega \\ 2\ \Omega \parallel 2\ \Omega &= 1\ \Omega \\ 12\ \Omega \parallel 4\ \Omega &= 3\ \Omega \\ 3\ \Omega + 3\ \Omega &= 6\ \Omega \\ 6\ \Omega \parallel 6\ \Omega &= 3\ \Omega \end{aligned}$$




$$I_1 = \frac{15}{1+3 \parallel 3} = \frac{15}{1+1.5} = 6\text{ A}$$

Using current division  
 $I = \frac{3}{3+3}(I_1) = 3\text{ A}$

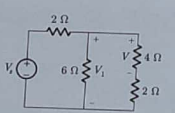**SOLUTION 2.42**


Correct answer is 10.  
The circuit can be simplified as  
 $3\ \Omega + 1\ \Omega = 4\ \Omega$   
 $4\ \Omega \parallel 4\ \Omega = 2\ \Omega$



Using voltage division  
 $V = \frac{4}{4+2}(V_s)$   
or  
 $4 = V_1 \left(\frac{4}{6}\right) \Rightarrow V_1 = 6\text{ volt}$

**Chapter 2**


Simplifying further we have

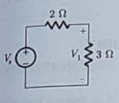


Using voltage division  
 $V_1 = \frac{3}{3+2}(V_s) \Rightarrow V_1 = \frac{5}{3} \times V_1 = 10\text{ volt}$

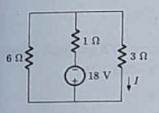**SOLUTION 2.43**

Correct answer is -4.  
The circuit can be reduced as shown below  
 $6\ \Omega + 2\ \Omega = 8\ \Omega$   
 $8\ \Omega \parallel 8\ \Omega = 4\ \Omega$   
 $4\ \Omega + 2\ \Omega = 6\ \Omega$



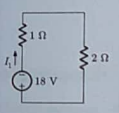Further simplifying  $6\ \Omega \parallel 3\ \Omega = 2\ \Omega$




$$I_1 = -\frac{18}{2+1} = -6\text{ A}$$

By current division  
 $I = \frac{6}{6+3}(-6) = \frac{6}{9}(-6) = -4\text{ A}$

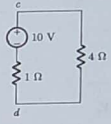
**SOLUTION 2.44**

Correct answer is 3.  
The circuit can be simplified as  
 $5 + 3 = 8\ \Omega$   
 $2 + 2 + 4 = 8\ \Omega$   
 $8\ \Omega \parallel 8\ \Omega = 4\ \Omega$



Using voltage division  $V_d = \frac{4}{4+5}(10) = 8\text{ V}$

We now work backward to get  $V_a$

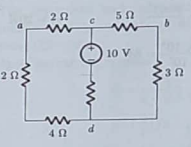

$$V_a = \frac{5}{5+3}(V_d) = \frac{5}{8} \times 8 = 5\text{ V} \quad (\text{Voltage division})$$

$$V_w = \frac{2}{2+2+4}(-V_w) = \frac{2}{8}(-8) = -2\text{ V} \quad (\text{Voltage division})$$

$$V_a = V_w + V_b = -2 + 5 = 3\text{ V}$$

**SOLUTION 2.45**

Correct answer is 4.

$$I_1 = \frac{18}{2} = 9\text{ A}$$

Current in  $4\ \Omega$  resistance is  $I_0 = kI_1$ . Power absorbed by  $4\ \Omega$  resistance

$$P = I_0^2(4) = k^2 I_1^2(4)$$

$$5184 = k^2(9)^2(4)$$

$$k^2 = 16 \Rightarrow k = 4$$

**SOLUTION 2.46**

Correct answer is 8.  
We have,  $V_s = 20R$   
Voltage across  $16\ \Omega$  resistance is  $V_{16\Omega} = 10V_s$   
Power absorbed by  $16\ \Omega$  resistor

$$P_{16\Omega} = \frac{(V_{16\Omega})^2}{16}$$

$$160 \times 10^3 = \frac{(10V_s)^2}{16}$$

$$160 \times 10^3 = \frac{(10 \times 20R)^2}{16}$$

$$R^2 = \frac{256 \times 10^4}{4 \times 10^4} = 64$$

$$R = 8\ \Omega$$

**SOLUTION 2.48**

Correct answer is 40.  
Applying KVL in the left most loop

$$V_1 - 10I_1 - 10I_1 = 0$$

$$I_1 = \frac{V_1}{20}$$

$$V_2 = -kI_1(10\ \text{k}\Omega \parallel 10\ \text{k}\Omega)$$

$$= -kI_1(5)$$


$$V_2 = -k\left(\frac{V_1}{20}\right)(5)$$

$$-4\left(\frac{V_2}{V_1}\right) = k$$

$$k = -4 \times (-10) = 40$$

**SOLUTION 2.49**

Correct answer is 48.

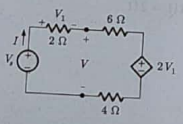

Applying KVL in the right half loop

$$V - 6I - 2V_1 - 4I = 0 \quad \dots(1)$$

Since  $V_1 = 2I$  (Ohm's Law)

Substituting  $V_1$  into equation (1), we have

$$V - 10I - 2(2I) = 0$$


$$I = \frac{V}{14} = \frac{42}{14} = 3\ \text{A}$$

KVL around the left half loop

$$V_s - 2I - V = 0$$

**SOLUTION 2.47**

Correct answer is 100.

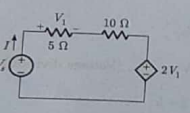

Power dissipated by  $5\ \Omega$  resistance

$$P = I^2 R$$

$$20 = (I)^2(5)$$

$$I = \sqrt{\frac{20}{5}} = 2\ \text{A}$$

KVL around the loop

$$V_s - 5I - 10I - 2V_1 = 0$$

$$V_s = 2(3) + 42$$

$$= 48\ \text{V} \quad (I = 3\ \text{A}, V = 42\ \text{V})$$

Applying KVL around the loop

$$30 + 0.4V_1 - 5I - 4 - 100I = 0$$

Since  $V_1 = 100I$  (Ohm's Law)

$$30 + 0.4(100I) - 5I - 4 - 100I = 0$$

$$30 + 40I - 5I - 4 - 100I = 0$$

$$26 - 65I = 0$$

$$I = 0.4\ \text{A}$$

Power absorbed by dependent source

$$P = -(0.4V_1)I \quad (\text{Passive sign convention})$$


$$= -(0.4)(100I)(I) \quad V_1 = 100I$$

$$= -40I^2$$

$$= -6.4\ \text{W}$$

**SOLUTION 2.50**

Correct answer is 7.

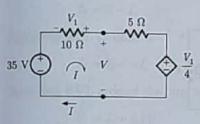

Applying KVL around the loop

$$35 - 10I - 5I - \frac{V_1}{4} = 0$$

Since  $V_1 = -10I$  (Ohm's Law)

$$35 - 15I - \left(-\frac{10I}{4}\right) = 0$$

$$35 - 15I + 2.5I = 0$$

$$I = \frac{35}{12.5} = 2.8\ \text{A}$$

Again, Applying KVL around the left half of the loop

$$35 - 10I - V = 0$$

$$V = 35 - 10I$$

$$= 35 - 10(2.8)$$

$$= 7\ \text{volt}$$

**SOLUTION 2.52**

Correct answer is 1.6.

The dependent and independent current sources are in parallel so they are replaced with a single current source of value  $(12 - 5I_1)$ .

Applying current division

$$I_1 = \frac{\frac{1}{3}}{\frac{1}{3} + \frac{1}{4} + \frac{1}{3}}(12 - 5I_1)$$


$$I_1 = \frac{2}{5}(12 - 5I_1)$$

$$5I_1 = 24 - 10I_1$$

$$I_1 = 1.6\ \text{A}$$


**SOLUTION 2.51**


Correct answer is -6.4.

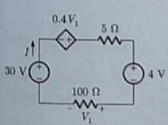


**SOLUTION 2.53**

Correct answer is 24.

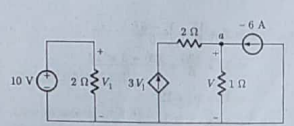

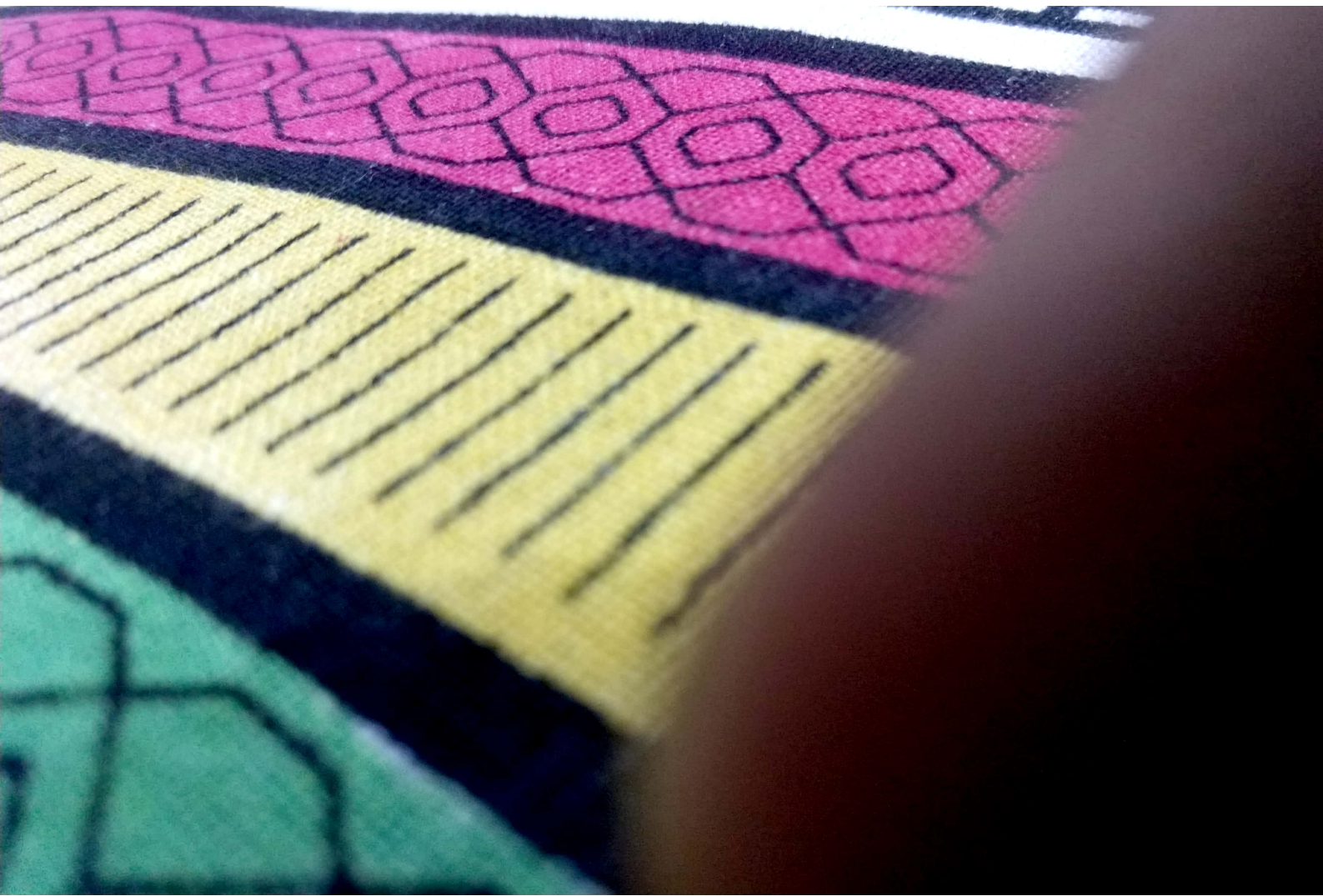

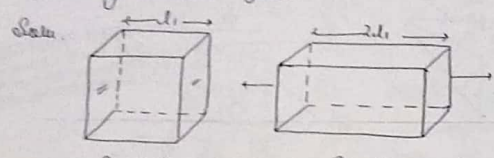Q. The resistance of cube shape material b/w any of its opp faces is  $2\Omega$  if this cube is stretched in 1 dir<sup>n</sup> by applying a linear force to double its original length then find the resist b/w 2 oppositely stretched faces.



$R_1 = 2\Omega$        $R_2 = ?$   
 $R_1 = \frac{\rho l_1}{a_1} = 2$        $R_2 = \frac{\rho_2 l_2}{a_2}$

$R_2 = \frac{\rho_2 (2l_1)}{a_2}$  (i)

$V_1 = V_2$

$l_1 a_1 = l_2 a_2$


$a_2 = \frac{l_1 a_1}{l_2} = \frac{l_1 a_1}{2l_1}$

ie  $a_2 = a_1/2$

$\rho_1 = \rho_2$   
 $\rho_1 l_1 = \rho_2 l_2$   
 $\frac{\rho_1 l_1}{a_1} = \frac{\rho_2 l_2}{a_2}$




$R_1 = R_2$

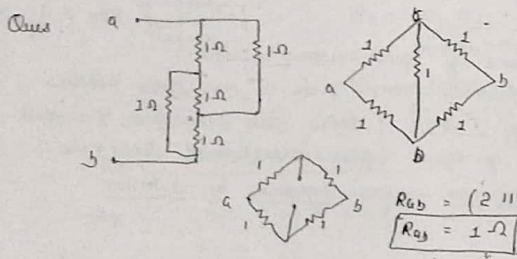so  $R_2 = \frac{\rho_2 (2l_1)}{(a_1/2)} = 4 \left( \frac{\rho_2 l_1}{a_1} \right) = 4 \times 2 = 8\Omega$





$R_{ab} = (2 || 2)$   
 $R_{ab} = 1\Omega$

Q.

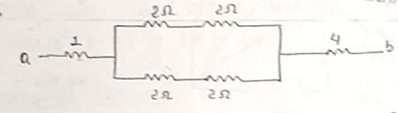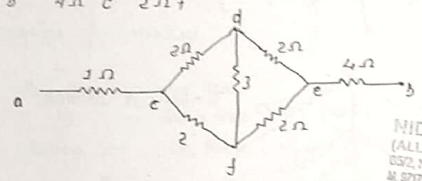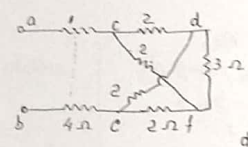



$R_{eq} = 1 + (4 || 4) + 4 = 1 + 2 + 4 = 7\Omega$

Q.

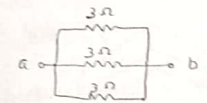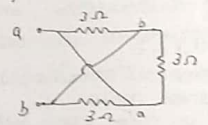



$R_{ab} = 3/3 = 1\Omega$

Ans.

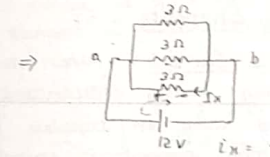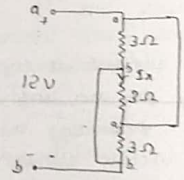


$i_x = \frac{-12}{3} = -4A$

Ans.

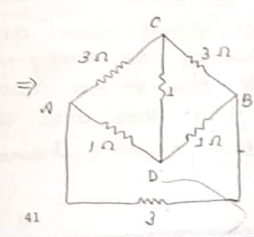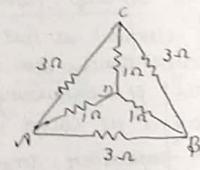

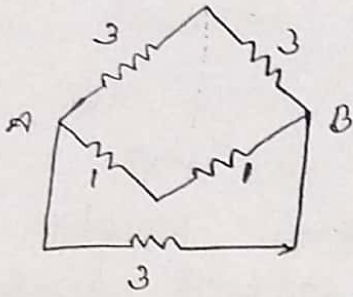
NIDHI PHOTOSTAT  
 (ALL NOTES AVAILABLE)  
 63/2, Nishi, Canal, Near Dabri-710016  
 M. 977920085, 9863457482, 9863215143






$$\begin{aligned}
 R_{AB} &= (6) \parallel 2 \parallel 3 \\
 &= 2 \parallel 2 \\
 &= 1
 \end{aligned}$$

Q.

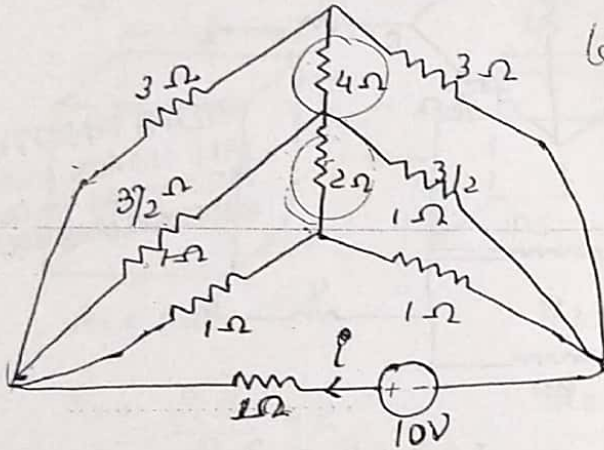

balanced bridge

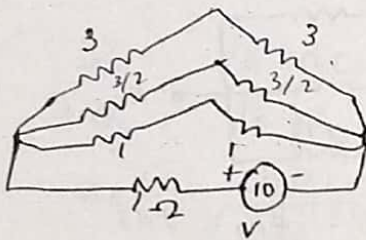+ve Res  $\rightarrow$  delivers P  
 $\rightarrow$  delivers P  
 -ve R  $\rightarrow$  absorbs P



$$\begin{aligned}
 R_{AB} &= 6 \parallel 3 \parallel 1 \parallel 2 \\
 &= 2 \parallel 2 \\
 R_{AB} &= 1 \Omega
 \end{aligned}$$

$$i = \frac{10}{1+1} = 5A$$

## Circuit Elements -

Active Element - When an element is capable of delivering energy independently for an infinite duration of time or capable of providing the power gain then element is called active element.


Eg - Vltz source, transistor, op-amp, current source.




Passive Element - When an element is not capable of delivering the energy independently for an  $\infty$  duration of time or not capable of providing the power gain then that element is called passive element. Eg. Resistor, Inductor, capacitor, XMR.

$$\frac{1}{R_{eq}} = \frac{1}{R} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

$$\frac{1}{R_{eq}} = \frac{n}{R}$$

$$R_{eq} = \frac{R}{n}$$

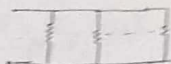

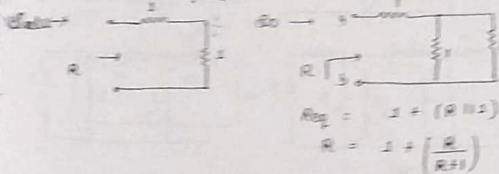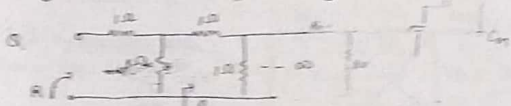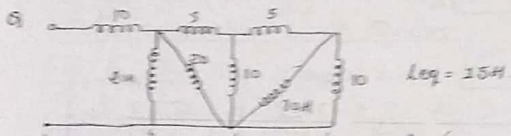

$$R_{eq} = 1 + (R || 1)$$


$$R = 1 + \left(\frac{R}{R+1}\right)$$

$$R^2 + R = R + 1 + R$$

$$R^2 - R - 1 = 0$$

$$R = \frac{-(-1) \pm \sqrt{1-4(-1)}}{2} = \frac{1 \pm \sqrt{5}}{2}$$

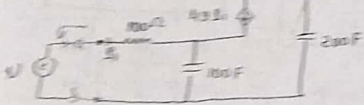
Q. Find equivalent cap. b/w terminals a & b



$$X = Z = R + sX_L - jX_C$$

$$= R + sL + \frac{1}{Cs}$$
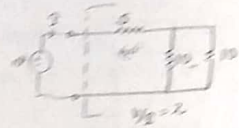
$$= 1R + \frac{1}{4} \frac{dI}{dt} + \frac{1}{Cs} \int i dt$$




$$V(s) = 100 I(s) + 50 I(s) \left(\frac{1}{(s/100)}\right)$$

$$\frac{V(s)}{I(s)} = 100 + \frac{5}{s}$$

$$Z(s) = 100 + \frac{5}{s} \text{ i.e. } R + \frac{1}{Cs}$$

$$V = 100 I_s + \frac{5}{100} \int 50 I_s dt$$

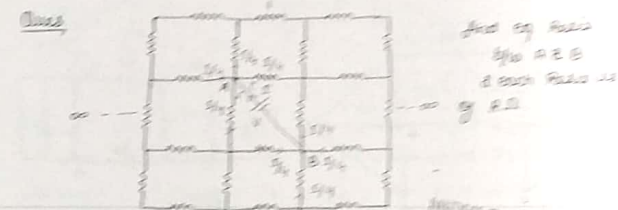
$$V = 100 I_s + \frac{1}{4} \int I_s dt$$



apply KVL  $\rightarrow -V + \frac{R}{4} + \frac{R}{4} = 0$   
 $V = R \left(\frac{R}{4} + \frac{R}{4}\right)$   
 $V/R = R_{th} = \frac{R}{2}$

Ques. Find eq. Ratio of b/w A & B when each edge has Ratio of R-0.

Solu-

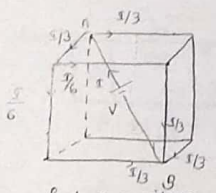


$$-V + \frac{V}{R \cdot 3} R + \frac{V}{6} R + \frac{V}{3} R = 0$$

$$V = I \left[ \frac{R}{3} + \frac{R}{6} + \frac{R}{3} \right]$$

$$\frac{V}{I} = \frac{5R}{6}$$

find Capacitance -

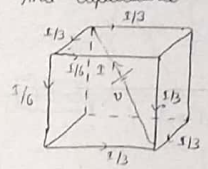




$$-V + \frac{1}{C} \int \frac{V}{3} dt + \frac{1}{C} \int \frac{V}{6} dt + \frac{1}{C} \int \frac{V}{3} dt = 0$$

$$V = \int I dt \left[ \frac{1}{3C} + \frac{1}{6C} + \frac{1}{3C} \right]$$

$$V = \int I dt \left[ \frac{5}{6C} \right]$$



$$V = \frac{1}{6/5 C} \int I dt$$

$$C_{eq} = \frac{6}{5} C$$

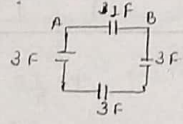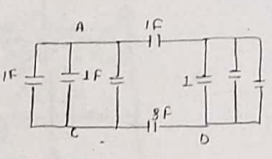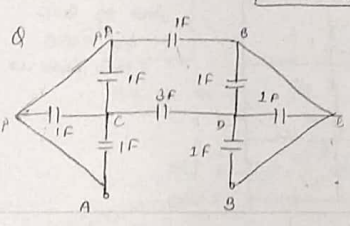


$$C_{eq} \Rightarrow \frac{1F}{1F} = 2F$$

Q. find equiv. Res. b/w terminal A & B

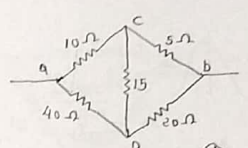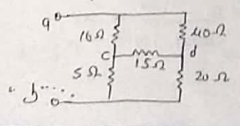

bridge  
 $10 \times 20 = 5 \times 40$

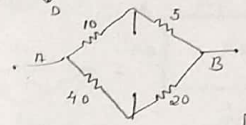


$$R_{ab} = 15 \parallel 60$$

$$= \frac{15 \times 60}{15 + 60}$$

$$R_{ab} = 12 \Omega$$

Condition for balanced bridge

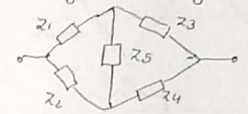- Product of resistance of opp arm should be equal
- $V_c = V_d$  &  $I_{CD} = 0$
- If impedances are there in bridge then it should satisfy both magnitude as well as angle condition.



$$Z_1 Z_4 = Z_2 Z_3$$

$$|Z_1| |Z_4| = |Z_2| |Z_3|$$

$$\theta_1 + \theta_4 = \theta_2 + \theta_3$$

Ques. If  $Z_1 = 10 \angle 30^\circ$ ,  $Z_2 = 5 \angle 50^\circ$ ,  $Z_3 = 4 \angle 40^\circ$  then for the bridge to be balanced find  $Z_4$

$$|Z_1| |Z_4| = |Z_2| |Z_3|$$

$$10 \angle 30^\circ \times Z_4 = 20$$

$$Z_4 = 2$$

$$30 + \theta_4 = -90 + (-40)$$

$$\theta_4 = -90 - 30$$

$$\theta_4 = -120$$

$$Z_4 = 2 \angle -120^\circ$$

$$= 2 \left[ \cos(120^\circ) - j \sin(120^\circ) \right]$$

$$= 2 \left[ -\frac{1}{2} - \frac{j\sqrt{3}}{2} \right] = (-1 - j\sqrt{3})$$

Real term  $\rightarrow$  -ve also can not